 


# ECE M116C - CA1 Report

## Datapath



The phases, from left to right, are Fetch, Decode, Execute, Memory, Register Write, Increase PC.

## Control Signal Table

Since my implementation aims to mimic the datapath described in class, the control signals are virtually the same as those in the week 2 discussion slides with some additions.

Instruction	Opcode	RegWrite	AluSrc	Branch	MemRead	MemWrite	MemtoReg	ALUOp
R-type	0110011	1	0	0	0	0	0	func
I-type	0010011	1	1	0	0	0	0	func
lw	0000011	1	1	0	1	0	1	ADD
sw	0100011	0	1	0	0	1	0	ADD
beq	1100011	0	0	1	0	0	0	SUB

All values are the same for BLT as they are for beq in the above table. Additionally, for JALR, the values in the 2nd column onwards are: 1100111, 1, 1, 1, 0, 0, 0, ADD.

## Questions

1. What is the total number of cycles for running “all” trace (ZERO instruction included)?

**13 cycles.**

2. How many r-type instructions does this program (“all”) have?

**2 r-type instructions (sub and add).**

3. What is the IPC of this processor (for “all” trace)?

**IPC = 1, simply because it performs one instruction per cycle.**